



IMPLEMENTATION OF KMAP BOOLEAN LOGIC WITH ARDUINO

L. Kiran Kumar Reddy

levaku.fwc1@iiitb.ac.in

COMETFWC027 IITB Future Wireless Communication (FWC) ASSIGNMENT

July 06, 2025

Abstract

The minimal sum-of-products expression for the logic function f represented by the given Karnaugh map is:

| PQ/RS | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 0 | 1 | 0 | 0 |
| 01 | 0 | 1 | 1 | 1 |
| 11 | 1 | 1 | 1 | 0 |
| 10 | 0 | 0 | 1 | 0 |

Options:

(A) $QS + \overline{P}R\overline{S} + PQR + \overline{P}RS + P\overline{Q}R$

(B) $QS + \overline{P}R\overline{S} + PQR + \overline{P}RS$

(C) $\overline{P}RS + PQR + \overline{P}RS + P\overline{Q}R$

(D) $\overline{P}RS + PQR + P\overline{Q}R$

Kmap

| PQ/RS | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 0 | 1 | 0 | 0 |
| 01 | 0 | 1 | 1 | 1 |
| 11 | 1 | 1 | 1 | 0 |
| 10 | 0 | 0 | 1 | 0 |

Components

| Component | Value | Quantity |
|---------------|-----------------------------|----------|
| Arduino Board | – | 1 |
| Jumper Wires | M-F | 10 |
| Push Buttons | – | 4 |
| Breadboard | – | 1 |
| USB Cable | – | 1 |
| LED | – | 1 |
| Resistors | 220 Ω , 10k Ω | 5 |

Setup

1. Connect buttons to pins D2–D5 for inputs P , Q , R , S , each with a 10k Ω pull-down resistor to ground.
2. Connect an LED to pin D13 through a 220 Ω resistor to ground.
3. Write Arduino code to read inputs and compute $f = !P \cdot R \cdot S + P \cdot Q \cdot R + !P \cdot R \cdot !S + !P \cdot Q \cdot R$.
4. Use `digitalWrite(13, f)` to control the LED based on the computed output.
5. Upload the code and test by pressing buttons to check when the LED turns ON for $f = 1$.

Implementation

Connect push buttons to pins D2–D5 for inputs P , Q , R , S with $10\text{k}\Omega$ pull-down resistors.

Connect an LED to pin D13 through a 220Ω resistor to ground.

Write Arduino code to read inputs and compute $f = !P \cdot R \cdot S + P \cdot Q \cdot R + !P \cdot R \cdot !S + !P \cdot Q \cdot R$.

Use `digitalWrite(13, f)` to control the LED based on the computed output.

Upload the code and test by pressing buttons to check when the LED turns ON for $f = 1$.